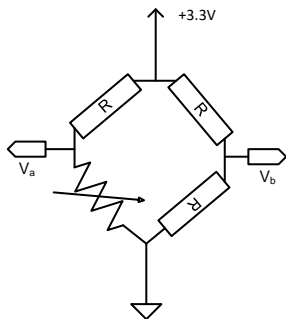


* Classic Wheatstone bridge



$$V_m = V_a - V_b$$

Advantages:

- Simple


Disadvantage:

- 2 analog inputs
- May be suitable if original voltage range is small

Conclusion:

Simplistic solution well suited if large voltage range.

* Wheatstone bridge with subtractor

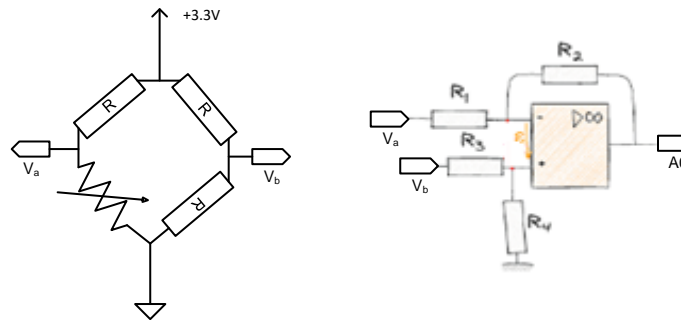

$$V_m = V_a - V_b$$

Advantages:

- One analog input


Disadvantage:

- + Complex

Conclusion:

More complex but well suited if voltage range small.

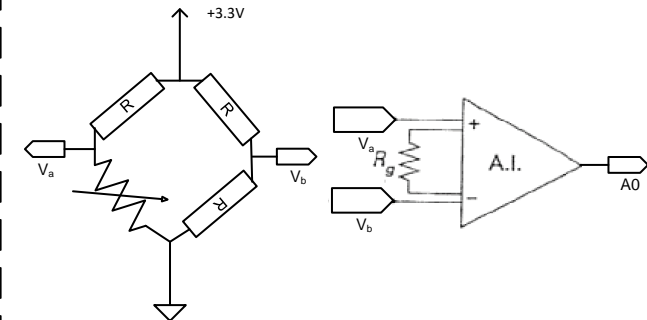* Wheatstone bridge with instrumentation amplifier



$$V_m = V_a - V_b$$

Advantages:

- 1 analog input
- If interference better (see next course)

Disadvantage:

- + Complex

Conclusion:

(see next course)

Conclusion:

In our case, the use of an instrumentation amplifier is perfect. It requires only one analog input, and allows better measurement of its value without interference.



Title : Wheastone bridge accompaniment

Author : PASCO Florian

Version: 001

Date: 02/28/2024

Page : 1/1

A4