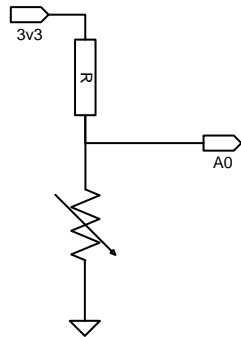


* Potentiometer mounting



Advantages:

- Simple
- Inexpensive


Disadvantage:

- Not always accurate enough

Conclusion:

To be preferred whenever possible, as it's simple and inexpensive, but may not be precise enough in some cases.

* Wheatstone bridge with thermistor

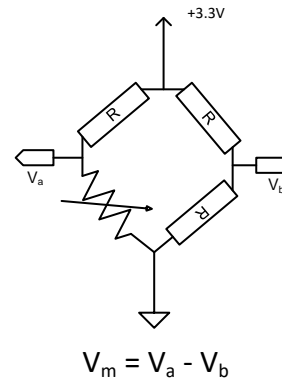

Advantages:

- Possibility of adding a gain in order to have a more relevant voltage range.


Disadvantage:

- + Complex

Conclusion:

Good solution if you have analog inputs and you're not satisfied with the voltage range provided by your transducer.

* Relaxation oscillator

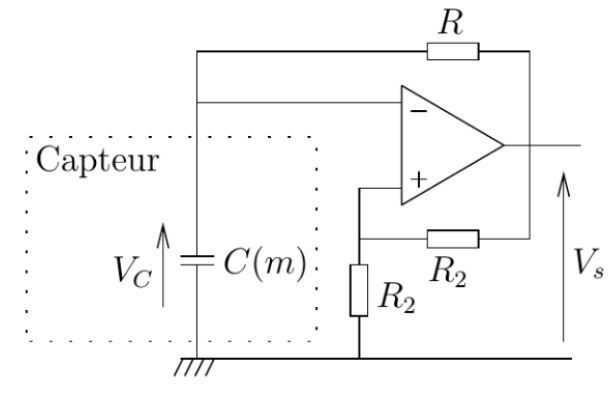

Advantages:

- Very useful if you don't have a DAC, as the output signal can be analyzed by a digital input.

Disadvantage:

- Requires very precise capabilities
- Requires an external power supply for -3.3V.

Conclusion:

Very useful if your microprocessor is not equipped with a DAC.

Conclusion:

In our case, the Wheatstone bridge seems the most appropriate, since the voltage range provided by our default sensor is unsatisfactory, we have a microcontroller equipped with analog inputs, and we don't have a high-precision capacitor.



Title : Thermistor Conditioning

Author : PASCO Florian

Version: 001

Date: 02/28/2024

Page : 1/1

A4